



HACETTEPE UNIVERSITY
COMPUTER ENGINEERING DEPARTMENT

BM233 LOGIC DESIGN LAB - 2020 FALL

FINAL PROJECT

January 31, 2021

Student name:
Şevval ATMACA

Student Number:
b21827115

1 Problem Statement

SCP-079 is an Exidy Sorcerer microcomputer built in 1978. SCP079 gained intelligence. Now, SCP-079 is trying to escape from the Foundation and destroy mankind. In this experiment, we design a verilog project using many scenarios what scp-079 like succeeds and fails.

2 State Diagram

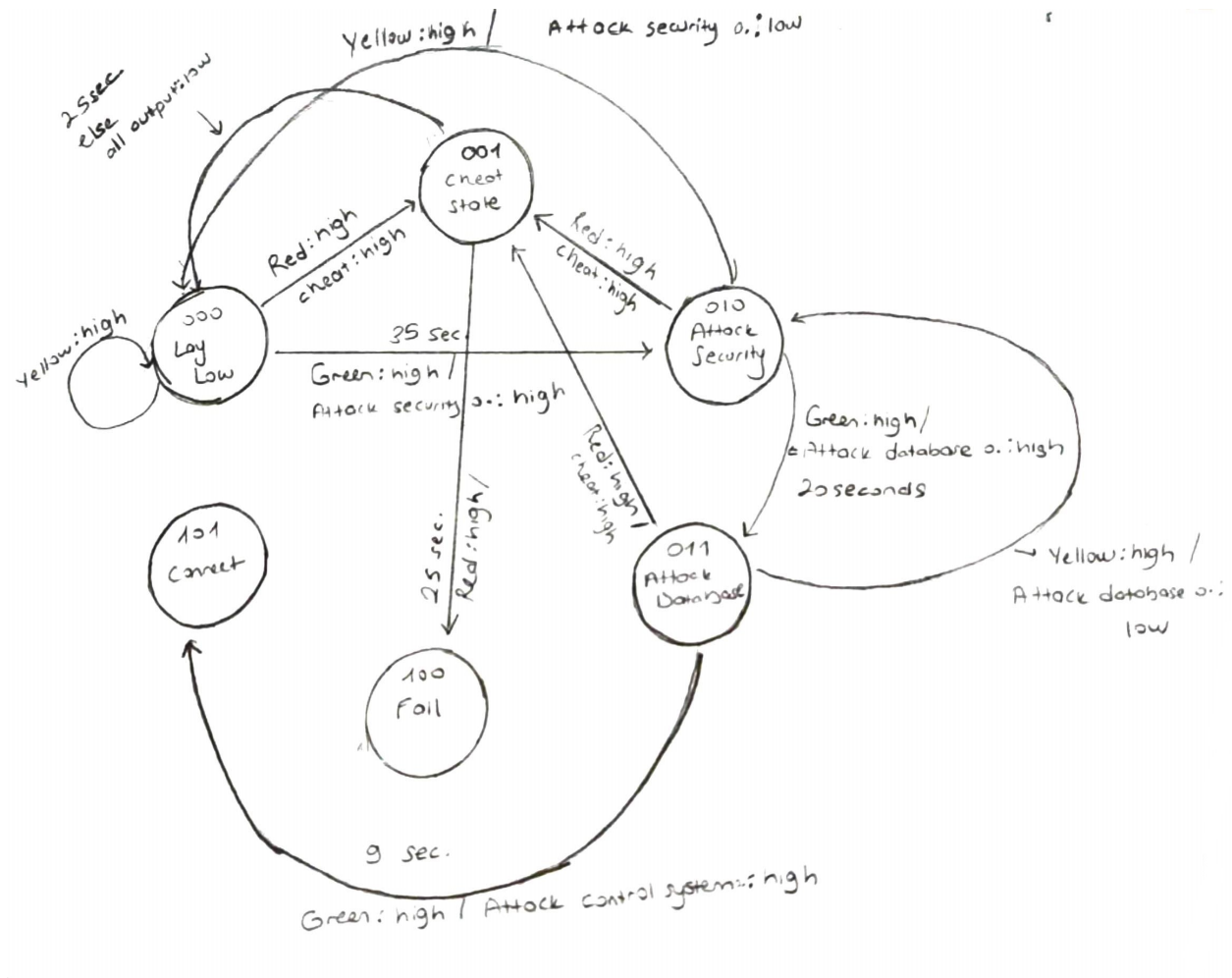


Figure 1: diagram

3 Codes

3.1 scp-079

```
1 module scp_079(  
2     input clock,  
3     input green,  
4     input yellow,  
5     input red,  
6  
7     output reg [2:0] state,  
8     output reg [5:0] timer ,  
9     output reg a1,  
10    output reg a2,  
11    output reg a3,  
12    output reg cheat_out  
13  
14 );  
15 /* a1:attack security output  
16    a2:attack database output  a3:control system output*/  
17  
18 reg [2:0] next_state;  
19  
20 reg cur_a1 = 0;  
21 reg cur_a2 = 0;  
22 reg cur_a3 = 0;  
23 reg cur_cheat = 0;  
24 /* I created "cur outputs" to change to outputs in correct time.*/  
25  
26 parameter s0= 3'b000, s1 = 3'b001, s2 = 3'b010,  
27            s3 = 3'b011, s4 = 3'b100, s5 = 3'b101;  
28  
29 /*s0:lay low   s1:cheat state  s2:attack security   s3:attack database  
30 s4:fail       s5:connect*/  
31  
32 always @(posedge clock) // always block to update state  
33     begin  
34         state <= next_state;  
35         timer <= timer + 1;  
36  
37         a1 = cur_a1;  
38         a2 = cur_a2;  
39         a3 = cur_a3;  
40         cheat_out = cur_cheat;  
41     end  
42  
43
```

```

44
45
46 always @(state, red, green, yellow, timer)begin
47     $display(state, red, green, yellow, timer , a1, a2, a3);
48     case(state)
49
50         s0 :
51             if(green == 1 & yellow == 0 & red == 0 & timer >= 6'b100011)
52                 begin next_state = s2; cur_a1 = 1; timer = 0;end
53
54             else if(red == 1)
55                 begin next_state = s1; cur_cheat = 1; timer = 0; end
56
57             else if(yellow == 1)
58                 begin next_state = s0; end
59
60
61         s1 :
62             if(red == 1 & timer >= 6'b011001)
63                 begin next_state = s4; timer = 0;end
64
65             else if( red != 1 & timer >= 6'b011001)
66                 begin next_state = s0; cur_a1 = 0; cur_a2 = 0;
67                 cur_a3 = 0; cur_cheat = 0; timer = 0;end
68
69
70
71         s2 :
72             if(yellow == 1 & red == 0)
73                 begin next_state = s0; cur_a1 = 0; timer = 0;end
74
75             else if(green == 1 & yellow == 0 & red == 0 & timer >= 6'b010100)
76                 begin next_state = s3; cur_a2 = 1; timer = 0;end
77
78             else if(red == 1)
79                 begin next_state = s1; cur_cheat = 1; timer = 0;end
80
81
82         s3 :
83             if(green == 1 & yellow == 0 & red == 0 & timer >= 6'b001001)
84                 begin next_state = s5; cur_a3 = 1; timer = 0;end
85
86             else if(red == 1)
87                 begin next_state = s1; cur_cheat = 1; timer = 0; end
88
89             else if(yellow == 1 & red == 0)
90                 begin next_state = s2; cur_a2 = 0; timer = 0; end
91

```

```
92         s4::;
93         s5::;
94
95         default : begin next_state = s0 ;timer = 1;
96         state = 3'b000; a1 = 0; a2 = 0; a3 = 0; cheat_out = 0;end
97     endcase
98 end
99 endmodule
```

3.2 alloc_{tb}

```
1
2
3 module alloc_tb;
4     reg clock;
5     reg green;
6     reg yellow;
7     reg red;
8
9     wire [2:0] state;
10    wire a1;
11    wire a2;
12    wire a3;
13    wire cheat_out;
14    wire [5:0] timer;
15
16    scp_079 UUT(.clock(clock), .green(green),
17    .yellow(yellow), .red(red), .a1(a1), .a2(a2), .a3(a3),
18    .cheat_out(cheat_out), .timer(timer), .state(state));
19
20
21    initial begin
22        clock = 0;#1;
23        forever begin
24            clock = ~clock;
25            #0.5;
26        end
27    end
28
29
30    initial begin
31        green=1;yellow=0;red=0;
32        #35;//0
33        #20;//2
34        #9;//3
35        #9;//5
36    $finish;
37    end
38 endmodule
```

3.3 a1trouble_{tb}

```
1
2  initial begin
3      clock = 0;#1; // for first 1 second, clock is 0
4      forever begin
5          clock = ~clock;
6          #0.5;
7      end
8  end
9
10 initial begin
11     green=1;yellow=0;red=0;
12     #35; //0
13     #6; //2
14     green=0;yellow=1;
15     #21; //0
16     green=1;yellow=0;red=0;
17     #14; //0
18     green=1;yellow=0;red=0;
19     #20; //2
20     #9; //3
21     #9; //5
22 $finish;
23 end
24
25 endmodule
```

3.4 a2trouble_{tb}

```
1
2  initial begin
3      clock = 0;#1;
4      forever begin
5          #0.5;
6          clock = ~clock;
7      end
8  end
9
10
11 initial begin
12     green=1;yellow=0;red=0;
13     #35; //0
14     #20; //2
15     #7; //3
16     yellow = 1; green = 0;
17     #1; //2
```

```

18         #21; //0
19         green=1; yellow=0; red=0;
20         #14; //0
21         #20; //2
22         #9; //3
23         #9; //5
24         $finish;
25     end
26
27 endmodule

```

3.5 cheatsuccess *tb*

```

1
2     initial begin
3         clock = 0; #1;
4         forever begin
5             #0.5;
6             clock = ~clock;
7         end
8     end
9
10    initial begin
11        green=1; yellow=0; red=0;
12        #35; //0
13        #6; //2
14        green=0; yellow=0; red = 1;
15        #12; //1
16        green=0; yellow=0; red=0;
17        #13; //1
18        #35; //0
19        green=1; yellow=0; red=0;
20        #20; //2
21        #9; //3
22        #9; //5
23        $finish;
24    end
25 endmodule

```


3.6 fail $_tb$

```
1
2     initial begin
3         clock = 0;#1;
4         forever begin
5             clock = ~clock;
6             #0.5;
7         end
8     end
9
10
11    initial begin
12        green=1;yellow=0;red=0;
13        #35;//0
14        #6;//2
15        green=0;yellow=0;red = 1;
16        #25;//1
17        #10;//4
18        $finish;
19    end
20 endmodule
```

4 Waveforms

4.1 alloc

- 1 In this scenario scp-079 was easily connected and succeeded.

 


Figure 2: alloc

4.2 a1trouble

- 1 In this scenario, scp-079 did some work and had to revert to its initial state,
- 2 but it still succeeded.

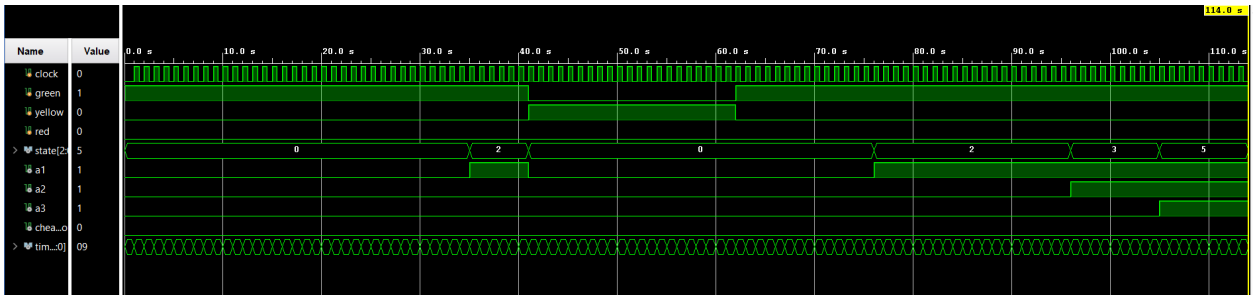


Figure 3: a1trouble

4.3 a2trouble

- 1 In this scenario, scp-079 tried harder this scenario than a1 situation, but it
- 2 still succeeded.

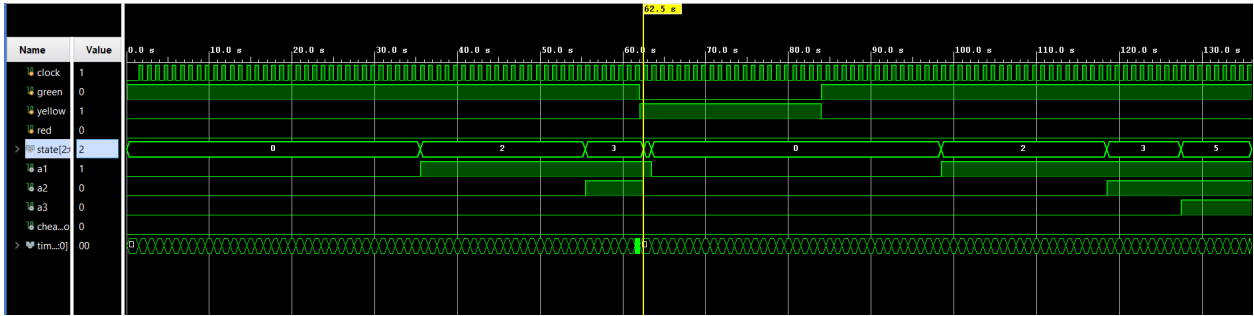


Figure 4: a2trouble

4.4 cheatsuccess

- 1 In this scenario scp-079 came to the cheat state but got rid of this state and
- 2 succeeded again.

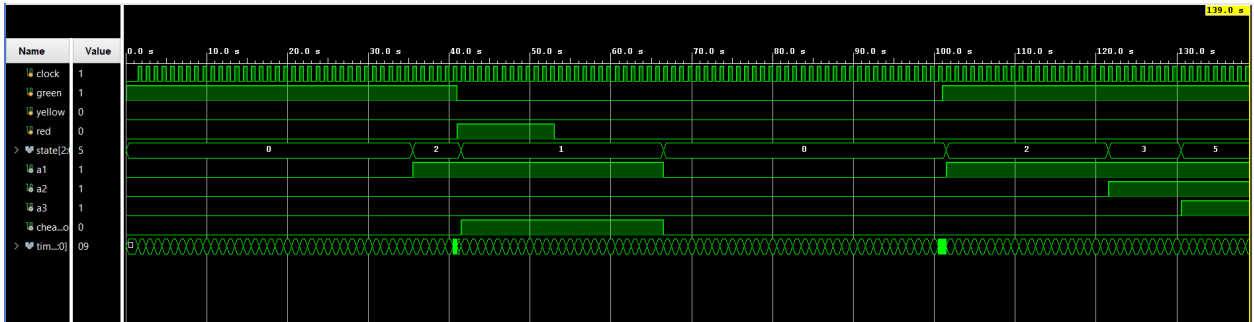


Figure 5: cheatsuccess

4.5 fail

```
1 In this scenario, Scp-079 came to the cheat state but could not come back
2 from here and the fail because it went to "fail_state".
```

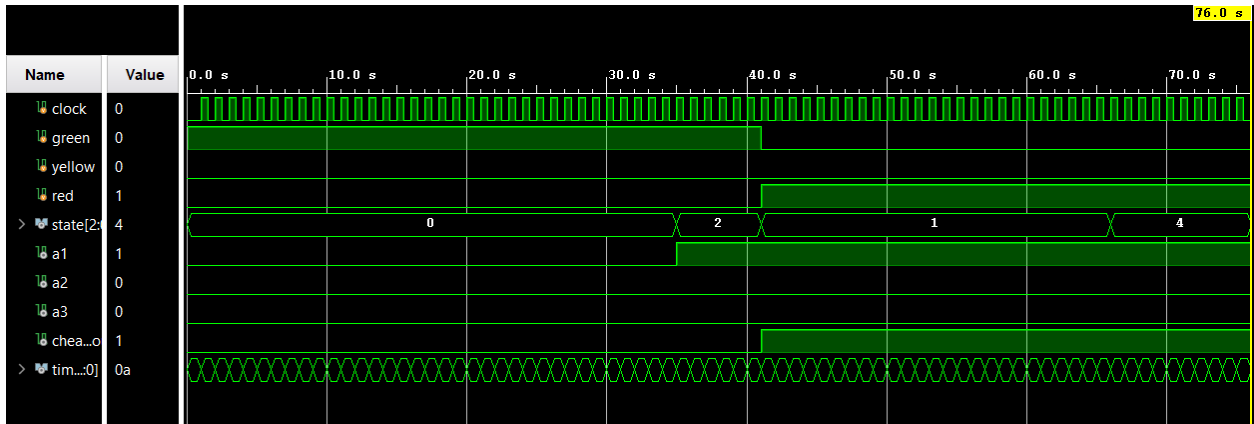


Figure 6: fail

References

- <https://www.xilinx.com/support/documentation/university/ISE-Teaching/HDL-Design/14x/Nexys3/Verilog/docs-pdf/lab10.pdf>
- <https://forums.xilinx.com/t5/Simulation-and-Verification/Change-simulation-time-behavioral-simulation-Vivado-2015-2/td-p/673373>
- https://www.xilinx.com/support/documentation/sw_manuals/xilinx2013_2/ug900-vivado-logic-simulation.pdf